

LAB 05 – COUNTER – 210495G – Nipun Viraj

- Task

We were assigned to do build a counter to represent a set of LEDs which take turns switching on and off either clockwise or anti-clockwise according to a button. We should use a D flip flop to determine the output of the next data set and also use a clock.

2. Completed Table

Q_t			Button	Q_{t+1}			D_2	D_1	D_0
Q_2	Q_1	Q_0		Q_2	Q_1	Q_0			
0	0	0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	1	0	0
0	0	1	0	0	1	1	0	1	1
0	0	1	1	0	0	0	0	0	0
0	1	1	0	1	1	1	1	1	1
0	1	1	1	0	0	1	0	0	1
1	1	1	0	1	1	0	1	1	0
1	1	1	1	0	1	1	0	1	1
1	1	0	0	1	0	0	1	0	0
1	1	0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0	0	0
1	0	0	1	1	1	0	1	1	0

k-Map for D_0

Q_0 Button \ $Q_2 Q_1$	$Q_2 Q_1$	$Q_2 Q_1$	$Q_2 Q_1$	$Q_2 Q_1$
	00	01	11	10
00	1	X	0	0
01	0	X	1	0
11	0	1	1	X
10	1	1	0	X

$$D_0 = Q_1 B + Q_2' B'$$

2. Completed Table

K-Map for D_1

$Q_2 Q_1 \backslash Q_0 B$	00	01	11	10
00	0	0	0	1
01	X	X	0	1
11	0	1	1	1
10	0	1	X	X

$$D_1 = Q_2 B + Q_0 B'$$

K-Map for D_2

$Q_2 Q_1 \backslash Q_0 B$	00	01	11	10
00	0	1	0	0
01	X	X	0	1
11	1	1	0	1
10	0	1	X	X

$$D_2 = Q_1 B' + Q_0' B$$

3. Design Sources

- 1. D Flipflop

```
entity D_FF is
    Port ( D : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC;
          Qbar : out STD_LOGIC);
end D_FF;

architecture Behavioral of D_FF is
begin
    process(Clk) begin
        if (rising_edge(Clk)) then
            if Res='1' then
                Q<='0';
                Qbar <= '1';
            else
                Q <= D;
                Qbar <= not D;
            end if;
        end if;
    end process;
end Behavioral;
```

3. Design Sources

- 2. Slowdown Counter

```
entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
           Clk_out : out STD_LOGIC);
end Slow_Clk;

architecture Behavioral of Slow_Clk is

    signal count: integer :=1;
    signal clk_status : std_logic :='0';

begin
    process (Clk_in) begin
        if (rising_edge(Clk_in)) then
            count <= count+1;
            if (count=5) then
                clk_status <= not clk_status;
                Clk_out <= clk_status;
                count <= 1;
            end if;
        end if;
    end process;
end Behavioral;
```

3. Design Sources

- 3. Counter

```
34 entity Counter is
35   Port ( Dir : in STD_LOGIC;
36         Res : in STD_LOGIC;
37         Clk : in STD_LOGIC;
38         Q : out STD_LOGIC_VECTOR (2 downto 0));
39 end Counter;
40
41 architecture Behavioral of Counter is
42
43   COMPONENT D_FF
44   PORT (
45     D : in STD_LOGIC;
46     Res : in STD_LOGIC;
47     Clk : in STD_LOGIC;
48     Q : out STD_LOGIC;
49     Qbar : out STD_LOGIC);
50   END COMPONENT;
51
52   COMPONENT Slow_Clk
53   PORT (
54     Clk_in : in STD_LOGIC;
55     Clk_out : out STD_LOGIC);
56   END COMPONENT;
57
58   signal D0,D1,D2 : std_logic;
59   signal Q0,Q1,Q2 : std_logic;
60   signal Clk_slow : std_logic;
61
62 begin
63
64   Slow_Clk0 : Slow_Clk
65   PORT MAP (
66     Clk_in => Clk,
67     Clk_out => Clk_slow);
```

```
66     Clk_in => Clk,
67     Clk_out => Clk_slow);
68
69   D0 <= (Q1 AND Dir) OR (NOT(Q2) AND NOT(Dir));
70   D1 <= (Q0 AND NOT(Dir)) OR (Q2 AND Dir);
71   D2 <= (Q1 AND NOT(Dir)) OR (NOT(Q0) AND Dir);
72
73   D_FF0 : D_FF
74   PORT MAP (
75     D => D0,
76     Res => Res,
77     Clk => Clk_slow,
78     Q => Q0);
79
80   D_FF1 : D_FF
81   PORT MAP (
82     D => D1,
83     Res => Res,
84     Clk => Clk_slow,
85     Q => Q1);
86
87   D_FF2 : D_FF
88   PORT MAP (
89     D => D2,
90     Res => Res,
91     Clk => Clk_slow,
92     Q => Q2);
93
94   Q(0) <= Q0;
95   Q(1) <= Q1;
96   Q(2) <= Q2;
97
98 end Behavioral;
99
```

4. Test Bench Codes

- 1. D Flipflop

```
) entity D_FF_Sim is
  -- Port ( );
end D_FF_Sim;

) architecture Behavioral of D_FF_Sim is
)
  COMPONENT D_FF
    PORT (D, Res, Clk : IN STD_LOGIC;
          Q, Qbar : OUT STD_LOGIC);
  END COMPONENT;

  SIGNAL D,Res,Clk : std_logic;
  SIGNAL Q,Qbar : std_logic;

  begin

)  UUT : D_FF PORT MAP(
    D => D,
    Res => Res,
    Clk => Clk,
    Q => Q,
    Qbar => Qbar);
)

  process
  begin
    Res <= '0';
    D <= '0';
    Clk <= '0';

    WAIT FOR 100ns;
```

```

    Res <= '1';
    Clk <= '0';

    WAIT FOR 100ns;

    Res <= '1';
    Clk <= '1';

    WAIT FOR 100ns;

    Res <= '0';
    D <= '1';
    Clk <= '0';

    WAIT FOR 100ns;

    Clk <= '1';

    WAIT FOR 100ns;

    Res <= '1';
    Clk <= '0';

    WAIT FOR 100ns;

    Res <= '1';
    Clk <= '1';

    WAIT;
  end process;
end Behavioral;
```


4. Test Bench Codes

- 2. Slow Down Counter

```
34 entity Slow_Clk_Sim is
35   -- Port ( );
36 end Slow_Clk_Sim;
37
38 architecture Behavioral of Slow_Clk_Sim is
39
40   COMPONENT Slow_Clk
41     PORT (Clk_in : IN STD_LOGIC;
42           Clk_out : OUT STD_LOGIC);
43   END COMPONENT;
44
45   SIGNAL Clk_in : std_logic;
46   SIGNAL Clk_out : std_logic;
47
48 begin
49
50   UUT: Slow_Clk PORT MAP (
51     Clk_in => Clk_in,
52     Clk_out => Clk_out);
53
54   process
55   begin
56     Clk_in <= '0';
57     WAIT FOR 20ns;
58     Clk_in <= '1';
59     WAIT FOR 20ns;
60     Clk_in <= '0';
61     WAIT FOR 20ns;
62     Clk_in <= '1';
63     WAIT FOR 20ns;
64     Clk_in <= '0';
65     WAIT FOR 20ns;
66     Clk_in <= '1';
67     WAIT FOR 20ns;
```

```
67     WAIT FOR 20ns;
68     Clk_in <= '0';
69     WAIT FOR 20ns;
70     Clk_in <= '1';
71     WAIT FOR 20ns;
72     Clk_in <= '0';
73     WAIT FOR 20ns;
74     Clk_in <= '1';
75     WAIT FOR 20ns;
76     Clk_in <= '0';
77     WAIT FOR 20ns;
78     Clk_in <= '1';
79     WAIT FOR 20ns;
80     Clk_in <= '0';
81     WAIT FOR 20ns;
82     Clk_in <= '1';
83     WAIT FOR 20ns;
84     Clk_in <= '0';
85     WAIT FOR 20ns;
86     Clk_in <= '1';
87     WAIT FOR 20ns;
88     Clk_in <= '0';
89     WAIT FOR 20ns;
90     Clk_in <= '1';
91     WAIT FOR 20ns;
92     Clk_in <= '0';
93     WAIT FOR 20ns;
94     Clk_in <= '1';
95     WAIT FOR 20ns;
96     Clk_in <= '0';
97     WAIT FOR 20ns;
98     Clk_in <= '1';
99     WAIT FOR 20ns;
100    Clk_in <= '0';
```


4. Test Bench Codes


- 3. Counter

```
34 entity Counter_sim is
35     -- Port ( );
36 end Counter_sim;
37
38 architecture Behavioral of Counter_sim is
39     COMPONENT Counter
40         PORT( Dir,Res,Clk : IN STD_LOGIC;
41             Q : OUT STD_LOGIC_VECTOR(2 downto 0));
42     END COMPONENT;
43
44     SIGNAL Dir,Res,Clk : std_logic;
45     SIGNAL Q : std_logic_vector(2 downto 0);
46
47     begin
48     UUT: Counter PORT MAP(
49     Dir => Dir,
50     Res => Res,
51     Clk => Clk,
52     Q=>Q
53     );
54
55     process
56     begin
57         Dir <= '0';
58         Res <= '1';
59         for i in 1 to 20 loop
60             Clk <= '0';
61             WAIT FOR 2 ns;
62             Clk <= '1';
63             WAIT FOR 2 ns;
64         end loop;
65         WAIT FOR 50 ns;
```

```
54
55     process
56     begin
57         Dir <= '0';
58         Res <= '1';
59         for i in 1 to 20 loop
60             Clk <= '0';
61             WAIT FOR 2 ns;
62             Clk <= '1';
63             WAIT FOR 2 ns;
64         end loop;
65         WAIT FOR 50 ns;
66         Res <= '0';
67         for i in 1 to 200 loop
68             Clk <= '0';
69             WAIT FOR 2 ns;
70             Clk <= '1';
71             WAIT FOR 2 ns;
72         end loop;
73         Dir <= '1';
74         WAIT FOR 50 ns;
75         for i in 1 to 200 loop
76             Clk <= '0';
77             WAIT FOR 2 ns;
78             Clk <= '1';
79             WAIT FOR 2 ns;
80         end loop;
81         WAIT;
82
83     end process;
84 end Behavioral;
```


4. Timing Diagrams

- 1. D Flipflop

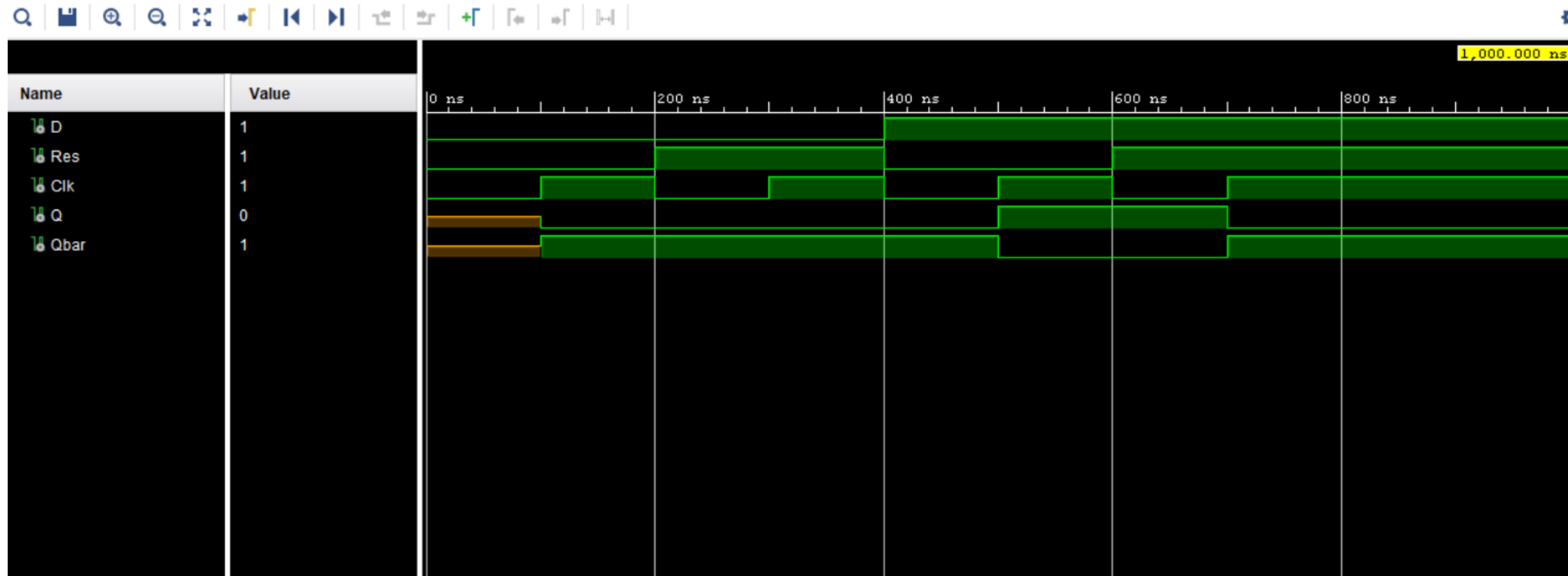


4. Timing Diagrams

- 2. Slowdown Counter

 

4. Timing Diagrams

- 3. Counter

 

5. Conclusions

We can build a counter circuit using VHDL behavioral modelling and high-level programming commands and the hierarchical design available. We also can even slow down the initial count rate according to our requirements using commands. Even the direction of counting can be controlled using a button in the Basys board.

Overall, we can say that VHDL behavioral modelling can be used to design complex sequential logic circuits.